



WEST BENGAL STATE UNIVERSITY
B.Sc. General Part-II Examination, 2020

ELECTRONICS
PAPER: ELTG-II

Time Allotted: 2 Hours

Full Marks: 50

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

Section-A

1. Answer any **five** questions from the following: 2×5 = 10
- (a) Draw the circuit diagram of half adder using NAND gates.
 - (b) Convert $(45)_{10}$ to binary equivalent number.
 - (c) What material do we use in the screen of CRO (Cathode Ray Oscilloscope)?
 - (d) What is meant by voltmeter sensitivity?
 - (e) What is the use of filters in the rectifier circuits?
 - (f) Define ripple factor. What is its value for a full-wave rectifier?
 - (g) Define percentage of regulation and efficiency of a rectifier.
 - (h) Can you construct an EX-OR gate using all NAND gates?
 - (i) What is Shunt regulator?

Section-B

Answer any four questions from the following 5×4 = 20

2. (a) What is MUX? Write down the truth-table of 4:1 MUX and draw its equivalent circuit using NAND gates only. (1+2)+2
- (b) Implement the following using 4:1 MUX
 $F(A, B, C) = \sum m(0, 2, 3, 5, 7)$
3. (a) Convert : (1+1+1)+2
- (i) $(1110111)_2$ into decimal
 - (ii) $(5129)_{10}$ into BCD
 - (iii) $(6F29AC)_{16}$ into binary
- (b) Subtract $(11)_{10} - (13)_{10}$ by using 2's complement method.

4. Implement the following function by using NAND gate: $A + AB + A\bar{B}C$. Convert $(2469)_{10}$ into BCD. 3+2
5. Design a D-flip flop using J-K flip flop. 5
6. (a) Simplify using Boolean algebra – $F(A, B, C) = ABC + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$ 3+2
(b) Differentiate combinational and sequential circuit.
7. (a) Convert a JK flip flop into T flip flop. 3+2
(b) Distinguish between Synchronous counter and Asynchronous counter.

Section-C

Answer any two questions from the following

10×2 = 20

8. (a) Draw the block diagram of successive approximation type DVM and explain its measurement method. 7+3
(b) Draw the circuit diagram of a Anderson bridge.
9. (a) What do you mean by Lissajous figures? 2+(3+2)+3
(b) Describe the deflection systems of CRO. What is the function of time base generator?
(c) Explain dual beam CRO.
- 10.(a) Draw the basic block diagram of an oscilloscope and explain the functions of each block. 6+(2+2)
(b) How is the vertical axis of an oscilloscope deflected? How does it differ from horizontal axis?
- 11.(a) Explain the working principle of square wave generator using IC-741 OP-AMP chip. 6+(2+2)
(b) Define the term duty cycle and time period of an oscillator.

N.B. : *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—×—